



EN: This Datasheet is presented by the manufacturer.

Please visit our website for pricing and availability at www.hestore.hu.

APPLICATION NOTE

Oscillators on 8-bit microcontrollers (2) AN97090

Abstract

“Going digital” and “programmable architectures” are the product strategies of today. However no digital system will run without a clock oscillator circuit and “oscillation” is an old and very analogue phenomena that may still need additional clarification. Quite some theory and some practice on this subject based on microcontrollers is covered in this application note.

© Philips Electronics N.V. 2001

All rights are reserved. Reproduction in whole or in part is prohibited without the prior written consent of the copyright owner.

The information presented in this document does not form part of any quotation or contract, is believed to be accurate and reliable and may be changed without notice. No liability will be accepted by the publisher for any consequence of its use. Publication thereof does not convey nor imply any license under patent- or other industrial or intellectual property rights.

APPLICATION NOTE

**Oscillators on 8-bit
microcontrollers
(2)
AN97090**

Authors:

**Andre Pauptit & Wim Rosink (*)
Philips Semiconductors Systems Laboratory Eindhoven,
The Netherlands**

Keywords:

crystals, overtone mode, transconductance, Pierce,
fundamental mode, 87C750, ceramic resonator.

Number of pages: 36

Date: 97-12-11 (*1st and final draft*), editing appendix: 2001-07-06 W.S.

Summary

Basically this application note is an addition to AN96103 "Xtal oscillators on 8-bit microcontrollers" It handles with harmonic Xtal resonation and ceramic resonators. Oscillator theory, component value calculations, parameter measurements is one part of this application note, application info with component type numbers is another part.

(*) Honourable mention

Wim Rosink

Wim Rosink retired this year after contributing more than 39 years to the Systems Lab Eindhoven. Wim has a long experience with many analogue circuits, like: oscillators in many variations, phase locked loops, etc.. This, combined with his knowledge on CMOS-technology and CMOS-digital families, makes him the ideal resource for the subjects of this application note. Most of the research and documenting for this application note was done by Wim.

The microcontroller sales support group is grateful to Wim for his high level contribution on the oscillator subject and is convinced that it will be useful to those that want or need more background on the oscillation issue in relation to microcontrollers.

Special thanks

A special thanks is given to muRata* and their representatives in Germany and the Netherlands for giving support by developing this application note.

(*TOYAMA MURATA MANUFACTURING CO., LTD)

CONTENTS

1. INTRODUCTION	6
1.1 The case	6
1.2 The subjects	6
2. OSCILLATION CONDITION AND CIRCUIT PARAMETERS.....	7
2.1 The crystal equivalent circuit	7
2.2 Equivalent circuit of the Pierce oscillator.	7
2.3 Design considerations for a Pierce oscillator.....	9
2.4 Drive level and power dissipation	10
2.5 Oscillator start-up time.....	10
2.6 Practical hints	11
3. TRANSCONDUCTANCE MEASUREMENT	12
4. XTAL CIRCUIT PARAMETERS.....	15
4.1 Measuring method	15
4.2 Measuring results.	16
5. CRYSTAL OVERTONE OSCILLATOR	17
5.1 Forcing overtone mode by frequency dependent damping.	18
5.2 Connection of a inductive trap filter to the output.	18
5.3 Inductive filter at the input.....	19
5.4 Drive level.	19
5.5 Conclusion.....	19
6. MURATA CERAMIC RESONATORS	21
6.1 Resonator types for 8400 and 8051 microcontrollers.....	21
6.2 Resonator types for the P87CL884	23
6.2.1 1...8 Mhz types	23
6.2.2 12...20 Mhz resonators.....	23
6.2.3 3.58 Mhz resonators.....	23
6.3 Resonator types for the P80C54/P87C51RA+	23
7. REFERENCES	24
APPENDIX.....	24

1. INTRODUCTION

Most microcontrollers include internal circuitry to generate the required clock pulses for the processor functions. The frequency rate of these clock pulses can be selected by some external components. For less demanding applications, simple LC circuitry or even an RC circuit can be used to fix the frequency. However, when a higher frequency stability is required, an oscillation circuit with a ceramic resonator or, for best stability, a circuit with external crystal should be used.

1.1 The case

Crystals are available for frequencies from 1MHz up to 100MHz and higher. For the higher clock frequencies, e.g. above 20 MHz, the resonators and crystals mostly will be used in a third or fifth overtone oscillation mode. This application note is basically build around one oscillator case with a microcontroller that runs on the higher frequencies also, so there is an opportunity to study behaviour of third overtone oscillation.

Fig.1 below shows this case, a typical circuit for a 39 MHz clock oscillator with a 39 MHz third overtone crystal and a P87C750 microcontroller.

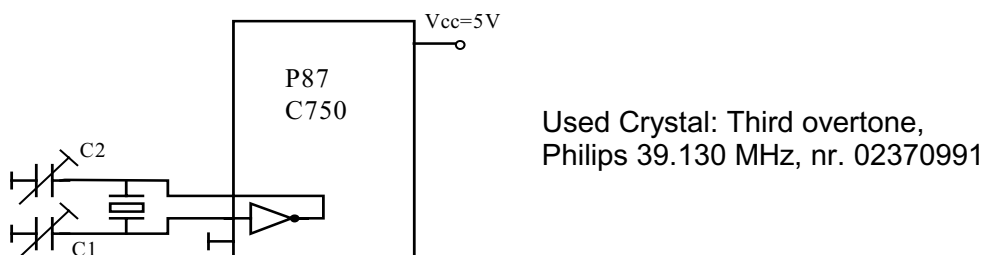


Fig.1 Pierce oscillator circuit

The crystal is connected directly to input and output of the microcontroller inverting gate. Two capacitors C_2 and C_1 are connected from these points to ground to perform the required load capacitance of the crystal. For most applications, the values of these capacitors are between 10 and 30pF and both about equal or $C_1 < C_2$. With $C_1 > C_2$, the feedback gain will be small, reducing the gate input voltage.

1.2 The subjects

The oscillation conditions are given by the crystal parameters, the external capacitors and the current gain or transconductance g_m of the inverter. The next two sections will describe following subjects:

- * how to calculate the oscillation condition ?
- * how to measure the crystal parameters ?
- * how to measure the oscillator gate circuit parameters ?

2. OSCILLATION CONDITION AND CIRCUIT PARAMETERS.

2.1 The crystal equivalent circuit

At the resonant point, the equivalent circuit of a crystal or resonator behaves like the circuit in Fig.2, hence a series connection of R_s , L_1 and C_a in parallel with capacitance C_b . The example shows a third overtone crystal with two main modes of resonance, one at $F_s = 13\text{MHz}$, the fundamental mode, and one at the third overtone mode at 39MHz . The circuit impedance is given by the equation below:

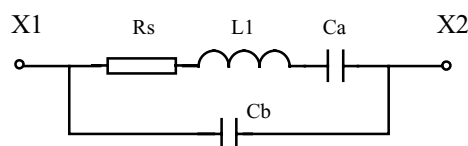


Fig.2 Equivalent crystal circuit.

$$Z_{XTAL} = \frac{1}{\frac{1}{R_s + j\omega L_1 + \frac{1}{j\omega C_a}} + \frac{1}{j\omega C_b}}$$

..... Eq.1

The values of the equivalent circuit components were measured with a impedance/phase analyser HP4194 for both resonance modes, as explained in section 4. The results are given in section 4.2:

Crystal electrical data of crystal:

Fundamental mode: $F_{s0} = 13.055\text{MHz}$ $R_s = 57\text{E}$, $C_a = 12\text{fF}$, $L_1 = 11.9\text{mH}$, $C_b = 2.8\text{pF}$

Third overtone: $F_{s3rd} = 39.13\text{MHz}$ $R_s = 30\text{E}$, $C_a = 1\text{fF}$, $L_1 = 16.8\text{mH}$, $C_b = 3.3\text{pF}$

In both modes, with the value of $C_b \gg C_a$, the “series resonance” frequency with F_s given by L_1 and C_a , will be very close to the value of the “parallel resonance” frequency, as given by L_1 and C_a, C_b in series, because $C_a C_b / (C_a + C_b)$ is close to C_a . Below it shows that a negative resistance has to be added to the circuit to compensate for the damping of R_s at oscillation by using the transconductance gain of the inverter for start up of the oscillator.

2.2 Equivalent circuit of the Pierce oscillator.

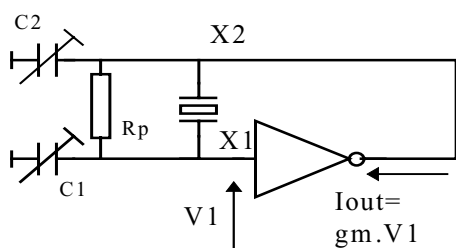


Fig.3a. Pierce oscillator circuit

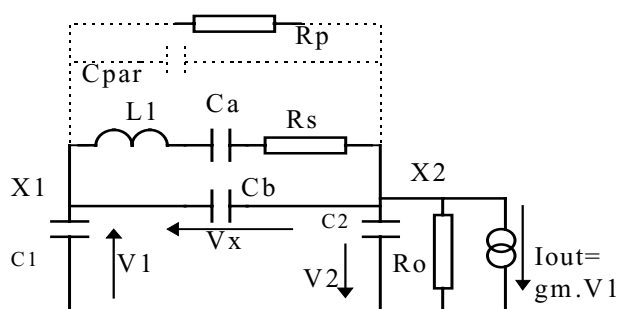


Fig.3b. Equivalent circuit

Fig. 3a+b shows the used Pierce oscillator circuit with its equivalent circuit diagram, in which the crystal is replaced by L_1, C_a, R_s and C_b . The inverter is replaced by its output impedance R_o and the output current from the transconductance gain: $I_{out} = g_m \cdot V_1$. R_p is a bias resistance to force the gate input to its threshold level to provide starting up. In most μ controller-types the feedback transistor R_p is already integrated as a semiconductor resistor parallel to the inverting gate.

In such a Pierce oscillator, the crystal should be operated in a “parallel resonance” mode with the parallel components C_b and $C1/C2$ in series. Therefore this circuit is also called the positive reactance oscillator, because the branch $L1/Ca/R_s$ should be inductive. At resonance, the total impedance is high, with a 180 degree phase shift between gate input and output signal.

The circuit will oscillate, if the negative reactance of the transconductance current gain just compensates for the damping of the resistive elements R_s , R_o and R_p .

A very convenient way and also rather easy to prove the oscillation condition is to transfer all these elements in series with R_s by means of the power dissipation rule, saying that the elements R_o , R_p and $g_m.V1$ are replaceable by a resistor in series with R_s , if this gives the same dissipation or damping to the circuit. Then the oscillation condition is true, if the total value of the resistive elements, including the own damping R_s of the crystal is less than zero.

After transferring all resistive elements into the series branch, the simplified resonance calculation model of fig. 4 can be used.

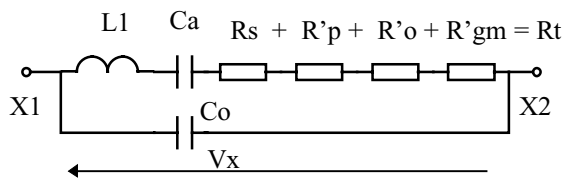


Fig.4 Resonance calculation model

$$C_o = C_b + C_{load} + C_{par.}$$

$C_{par.}$ = parasitic capacitance across gate.

$$C_{load} = C1C2 / (C1 + C2)$$

$C1, C2$ include parasitics at input and output.

At resonance with $C_o \gg C_a$, $\omega_o = 1/\sqrt{L1.C_a}$

$$R_t = R_s + R'_p + R'_o + R'_{gm}$$

In this figure, C_o is the total parallel capacitance, including load capacitance C_{load} formed by the capacitance's $C1$ and $C2$ in series and the parasitic capacitance's at input and output and in parallel with the gate. The value of R_t is given by $R_t = R_s + R'_p + R'_o + R'_{gm}$.

Assuming that in resonance, $I_{R_t} = I_{C_o}$, then it follows for R'_p :

$P_{R_p} = P'_{R_p}$, or $(V_x)^2/R_p = I_{R_t}^2 \cdot R'_p$ or with $I_{R_t} = I_{C_o} = (V_x) \cdot \omega_o \cdot C_o$ it follows:

$$(V_x)^2/R_p = V_x^2 \cdot \omega_o^2 \cdot C_o^2 \cdot R'_p \quad \text{or...}$$

$$R'_p = \frac{1}{\omega_o^2 \times C_o^2 \times R_p} \quad \text{.....Eq.2}$$

For the output impedance R_o follows with $P_{R_o} = P'_{R_o}$:

$V_2^2 / R_o = I_{R_o}^2 \cdot R'_o$, or with $V_2 = V_x \cdot C1/(C1+C2)$ and $I_{R_o} = I_{C_o} = V_x \cdot \omega_o \cdot C_o$ it follows:

$$V_x^2 \cdot C1^2 / (C1+C2)^2 / R_o = V_x^2 \cdot \omega_o^2 \cdot C_o^2 \cdot R'_o \quad \text{or...}$$

$$R'_o = \frac{1}{\omega_o^2 \times C_o^2 \times R_o} \times \frac{C1^2}{(C1+C2)^2} \quad \text{.....Eq.3}$$

Transferring $I_o = g_m \cdot V1$ to R'_{gm} means, with $P(g_m.V1) = P_{R'_{gm}}$:

$-g_m \cdot V1 \cdot V2 = I_{R_t}^2 \cdot R'_{gm}$, or with $V1 = V_x \cdot C2/(C1+C2)$, $V2 = V_x \cdot C1/(C1+C2)$ and $I_{R_t} = I_{C_o}$ it follows:

$$-g_m \cdot V_x^2 \cdot C1 \cdot C2 / (C1+C2)^2 = V_x^2 \cdot \omega_o^2 \cdot C_o^2 \cdot R'_{gm} \quad \text{or...}$$

$$R'_{gm} = \frac{-g_m}{\omega_o^2 \times C_o^2} \times \frac{C_1 \times C_2}{(C_1 + C_2)^2} \dots\dots\dots \text{Eq.4}$$

Combining these equations, we obtain for the total series resistance:

$$R_t = R_s + \frac{1}{\omega_o^2 C_o^2} \left(\frac{1}{R_p} + \frac{1}{R_o} \left(\frac{C_1}{C_1 + C_2} \right)^2 - g_m \frac{C_1 C_2}{(C_1 + C_2)^2} \right) \dots\dots\dots \text{Eq.5}$$

The circuit will oscillate, if the value of R_t is zero or negative. So the minimum value of g_m should be:

$$g_m \geq R_s \times \frac{\omega_o^2 C_o^2 (C_1 + C_2)^2}{C_1 C_2} + \frac{1}{R_p} \frac{(C_1 + C_2)^2}{C_1 C_2} + \frac{1}{R_o} \frac{C_1}{C_2} \dots\dots\dots \text{Eq.6}$$

The first two products of this equation are reduced to a minimum value with $C_1 = C_2$. This means, that for easiest oscillation, both load capacitance's should be equal. In this case we find:

$$g_{m.\min} \geq R_s \times 4\omega_o^2 C_o^2 + \frac{4}{R_p} + \frac{1}{R_o} \dots\dots\dots \text{Eq.7}$$

The last equation for the minimum required value for g_m confirms quite well with the values as derived in the publications as mentioned in references 3 and 4. To determine $g_{m.\min}$ for worst case design, it should be noted, that the value of R_s may vary with the drive level, and can be much higher than the specified value from device data at low drive level during start-up. See also section 2.6.

Ref.4. from Rusznyak also derives a maximum value for the transconductance, above which oscillation is not possible. In most cases this value is much higher than the minimum value and can be neglected. However for low frequency crystals, operating around 16 to 32 kHz, it might be of influence for the oscillation condition. The equation for this maximum allowable value for the transconductance is, with $C_p = C_b + C_{par}$, see fig.(3+4) :

$$g_{m.\max} \leq \frac{1}{R_s} \times \frac{C_1 C_2}{C_p^2} \dots\dots\dots (\text{Rusznyak}) \dots\dots\dots \text{Eq.7a}$$

2.3 Design considerations for a Pierce oscillator.

Based upon equation 7, a first estimation can be made about the oscillation condition for a certain combination of inverter gate and crystal. As an example we take the third overtone crystal as mentioned in the example above and the gate of a P87C750 microcontroller of which measured data are given in section 4.2, as crystal NR. 7.

The crystal electrical data:

Fundamental mode:	Fs0=13.055MHz	Rs=57E, Ca=12fF, L1=11.9mH, Cb=2.8pF
Third overtone:	Fs3rd=39.13MHz	Rs=30E, Ca=1fF, L1=16.8mH, Cb=3.3pF

From the measurements in section 3 for the inverter gate it follows:

Transconductance $g_m = 2$ to 5 mA/V (typical, not worst case!), output impedance $R_o = 3000 \Omega$
Bias resistance $R_p = >1 \text{ M}\Omega$.

Then with $C_o = C_b + C_{load} + C_{par} = 10\text{pF}$ and $C_1 = C_2$, with eq.7 the minimum value for g_m should be:

Fundamental: $\omega_o.C_o = 0.000820$ and $g_{m.\min} = 0.000153 + 0.000004 + 0.00033 = 0.000487 \text{ S.}$

Third overtone: $\omega_0 C_0 = 0.00246$ and $g_{m-\min} = 0.000725 + 0.000004 + 0.00033 = 0.001059$ S.

Hence for both modes, with $g_{m-\min} = 0.002$ S, the circuit will oscillate. To suppress the not wanted fundamental mode, special measures are required, as using an inductive trap filter or using extra damping across the circuit. This subject will be described in more detail in section 5.

From Eq.7 it can be derived, that with given g_m and R_0 , and with $R_p \gg 4R_0$ the maximum value of the parallel capacitance C_0 of the crystal is inversely proportional with the root value of R_s , or

$$C_0^2 \leq \frac{g_m - 1/R_0}{4\omega_o^2 R_s} \dots \text{or} \dots C_0 \leq \frac{1}{2\omega_o} \sqrt{\frac{g_m - 1/R_0}{R_s}} \dots \text{Eq.8}$$

For the crystal above at $F_s = 39\text{MHz}$, $R_0 = 3000\Omega$, $R_s = 30\Omega$ and $g_m = 1\text{mA/V}$, we find $C_0 < 9.6\text{ pF}$.

With $R_s = 100\Omega$, $C_0 < 5.2\text{ pF}$, with $R_s = 10\Omega$, the allowed value for $C_0 = < 16.7\text{ pF}$.

From the values shown the conclusion will be, that for a 30MHz overtone crystal, the value of the load capacitance's are rather limited. With C_0 being below 10pF, proper values for C_1 and C_2 are also below 10pF.

2.4 Drive level and power dissipation

For most crystals a maximum drive level is specified, e.g.. $< 5\text{mW}$. The drive level can be calculated from the power dissipation in the series resistance R_s of the crystal. At resonance, the power dissipation is: $P_d = I_{Rt}^2 \cdot R_s$, with $I_{Rt} = V_x \cdot \omega_0 \cdot C_0$ and V_x as the effective voltage across the crystal. At resonance the voltages across the crystal at points X1 and X2 are opposite in polarity and the maximum peak to peak value for both is about the supply voltage V_{cc} . Hence the effective value V_x across V_{C0} is $V_{cc}/\sqrt{2}$ or $V_x = 3.5\text{V}$. So we find $P_d = (3.5 \omega_0 C_0)^2 \cdot R_s$, or

$$\text{Drive level} \dots P_d = 483 \times f_s^2 \times C_0^2 \times R_s \dots \text{Eq.9.}$$

With the crystal from before at $f_s = 39\text{MHz}$, $C_0 = 10\text{pF}$ and $R_s = 30\Omega$, we get: $P_d = 0.0022\text{ Watt}$.

For applications requiring high stability, databooks advise drive levels between $5\text{ }\mu\text{W}$ and 1 mW .

- Drive levels above 5 mW may seriously affect the frequency stability of the quartz crystal.

- Resonators are much less sensitive for overdrive, they can be used at higher drive levels.


Special attention should be taken with crystals, operating in the overtone mode at high frequencies far above 10MHz, because of the square influence of the resonance frequency on P_d , see Eq.9.

E.g.. for the A216 crystal, see section 4.2, nr.10., with $F_s = 35.25\text{MHz}$, $R_s = 69\Omega$ and $C_0 = 20\text{pF}$, $P_d = 16.6\text{ mW}$.

For this case, the load C_0 should be reduced to a lower value, e.g. 10pF . Then, $P_d = 4.1\text{mW}$.

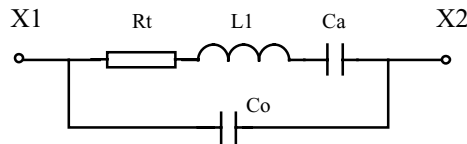2.5 Oscillator start-up time

With the fundamental resonance model as shown in Fig.4, the oscillation start-up time can be calculated by assuming an initial noise current through the circuit and $V_{C0} = V_{in}$ at $t=0$.



Then by using Laplace transformation, for the voltage across Co it can be derived:

$$V_{Co} = V_{in} \times e^{-\alpha t} \sin \omega_o t, \text{ with } \alpha = R_t / 2L_1 \text{ and } \omega_o \cong 1/\sqrt{L_1 C_a} \dots\dots\dots \text{Eq.10}$$

To assure, that the voltage V_{Co} increases, R_t should be negative, with a sufficient high value of g_m . Then, for each $\Delta t = 1/\alpha$, V_{Co} increases with a factor $e=2.72$. Hence, to increase V_{Co} from its initial noise level of e.g.. $1\mu V$ to a logic level of 2.5V, for start up it will take:

$$T_{\text{start-up}} = \ln(2.5/1e-6) = 15 \times 1/\alpha \text{ sec.} \dots\dots\dots \text{Eq.11}$$

The value of R_t is given by Eq.5. Neglecting part $1/R_p$ with $4/R_p \ll 1/R_o$ and $C_1=C_2$, it follows:

$$R_t = R_s + \frac{1}{4\omega_o^2 C_o^2} \left(\frac{1}{R_o} - g_m \right) \dots\dots\dots \text{Eq.12}$$

Some examples:

Crystal nr.7, $F_s=39\text{MHz}$, $C_o=10\text{pF}$, $g_m=0.002\text{mA/V}$, $R_o=3000\Omega$, $R_s=30\Omega$, $L_1=16.8\text{mH}$..

$R_t=30 + 1/0.000024(1/3000 - 0.002) = 30 - 69 = -39\Omega$. Hence $\alpha = R_t/2L = 1160.\text{sec}^{-1}$.

So the start up time from $1\mu V$ to 2.5V amounts $T_{\text{startup}} = 15 \times 1/1160 = 0.013 \text{ sec}$.

Crystal nr.4, $F_s= 32\text{kHz}$, $C_o= 20\text{pF}$, $L_1=9.3\text{kHz}$, $R_s=15$ to $50\text{k}\Omega$ (from data)

For this type, g_m should be reduced to keep its value below $g_{m,\text{max}}$ as given in Eq.7a.

From this equation we get $g_{m,\text{max}} = 1/R_s \times (C_1/C_o)^2 = < 100\mu S$..

Further $g_{m,\text{min}} = R_s \cdot 4\omega_o^2 C_o^2 = 15e3 \cdot 4 = 1\mu S$. Assume $g_m = 15\mu S$ and $R_o=3.8\text{M}\Omega$, as given in the micro controller data handbook, IC20. Hence, $R_t = 15e3 + (1/64e-12)(1/3.8e6 - 15e-6) = 15e3 + 4100 - 234e3 = 215e3 \Omega$.

So $R_t/2L=11.6 \text{ sec}^{-1}$, and the start-up time $T_{\text{startup}} = 15 \times 1/11.6 = 1.3 \text{ sec}$.

2.6 Practical hints

- Testing : Do not use probe at gate input side, this will disturb biasing level.
- At higher frequencies, the load capacitance's C1 and C2 need to be lower to limit drive level, e.g.. for a 30 MHz overtone crystal, with $R_s=30\Omega$, $C_1=C_2 = <10 \text{ pF}$.
- With $C_1 < C_2$, the circuits power consumption will be reduced. Higher input signal means higher dV/dT and shorter operation in threshold region.
- For most micro controllers, the signal at the input of the oscillator gate is also used for the internal clock. Therefore take $C_1 < C_2$ to assure that the input level is sufficient high.
- For a third or fifth overtone crystal, use a tank filter to suppress the fundamental mode.
- For high frequency ceramic resonators operating in overtone mode, in general no filter is required, these components have build in measures to suppress unwanted frequencies.
- When calculating the minimum required value of the transconductance g_m for start-up, take care that due to the drive level dependency, the value of the serial resistance R_s of the crystal at start-up may be much higher, from 10% higher up to ten times the specified or measured value at operating condition.

3. TRANSCONDUCTANCE MEASUREMENT

The XTAL oscillators, described in this note are of the type Pierce and operate with the internal inverter stage of the microcontroller. For calculations, such a gate amplifier can be replaced in the simulation circuit with one of the simplified diagrams of Fig.5.

In the current source equivalent, the output current I_o is defined by the transconductance g_m of the gate and the input voltage V_{in} as: $I_o = g_m \times V_{in}$. For a CMOS gate as used here the input resistance R_i can be neglected. In most cases, the output impedance R_o is much higher than the output load resistance and the output can be seen as a real current source with $I_o = g_m \cdot V_{in}$.

In the voltage source equivalent, the current source is replaced by a voltage source $e_o = g_m \cdot V_{in} \cdot R_o$. Again, with $R_o \gg R_{load}$, the output behaves as a current source, $g_m \cdot V_{in}$.

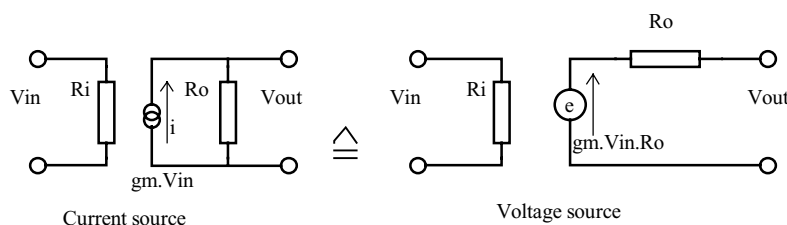


Fig. 5. Gate equivalent circuit

Fig.6 shows a standard test set up to measure the transconductance of the CMOS gate, as used for CMOS products like the HCU04. With a fixed input voltage at 100kHz, V_{out} was measured and then the transconductance can be calculated as:

$$g_m = \frac{I_o}{V_{inp}} = \frac{V_{out}}{R_l \times V_{inp}} \dots \dots \dots \text{Eq.13.}$$

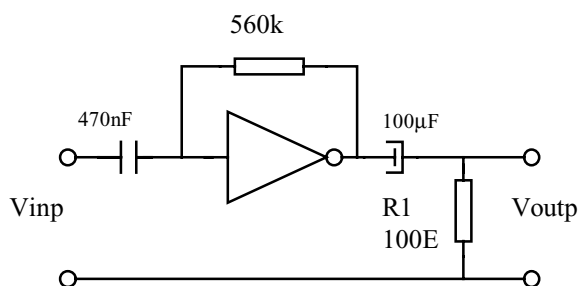


Fig.6 Test circuit transconductance

Test results with some microcontroller devices and the calculated values for the transconductance are listed in the following table.

TABLE 1 $V_{inp}=400\text{mV}$ at 100kHz , $R_I=100\Omega$.

Device:	$V_{cc}=5\text{V}$		$V_c=4\text{V}$		$V_{cc}=3\text{V}$	
	V_{out}	g_m	V_{out}	g_m	V_{out}	g_m
P87C750, EBFFA,16	200 mV	5 mA/V	180 mV	4.5 mA/V	120 mV	3 mA/V
P87C750, PBFFA,40	200 „	5 „	170	4.25 „	100 „	2.5 „
EP87C750-4N	180 „	4.5 „	150 „	3.75 „	100 „	2.5 „
P87C750 EBPN	210 „	5.25 „	170 „	4.25 „	120 „	3 „
S87C751 4F24	130 „	3.25 „	100 „	2.5 „	60 „	1.5 „
P87C748 EBFFA	200 „	5 „	160 „	4 „	100 „	2.5 „
P87C750 PBFFA	200 „	5 „	150 „	3.75 „	100 „	2.5 „

The table shows, that at $V_{cc}=5\text{V}$, the transconductance amounts 3 to 5mA/V . At $V_{cc}=3\text{V}$, a minimum value of $g_m=1.5\text{mA/V}$ was found, so for calculation, use $g_{m-\min}=1\text{mA/V}$.

The value of the output impedance R_o may influence the effective value of g_m if not $R_o \gg R_{load}$. Therefore the value of R_o was also measured with the test circuit Fig.7.

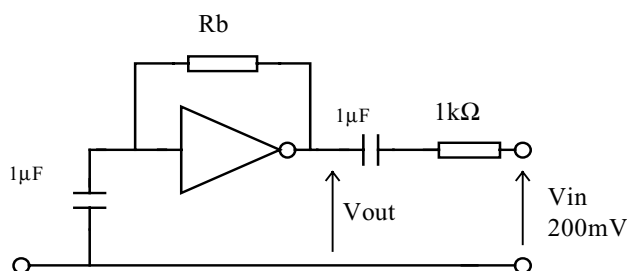


Fig.7 Test circuit output impedance

A signal V_{in} is supplied to the output of the gate via a $1\text{k}\Omega$ series resistance and a decoupling capacitor of $1\mu\text{F}$. The gate input is kept quiet by a capacitor to ground to prevent any input signal passing from the output through R_b . With $R_b \gg 1\text{k}\Omega$ it follows:

$$\frac{V_{in}}{V_{out}} = \frac{1000 + R_o}{R_o}, \text{ or } R_o = 1000 \left(\frac{V_{out}}{V_{in} - V_{out}} \right) \dots\dots\dots \text{Eq.14}$$

With $V_{in} = 200\text{mV}$ at 100kHz , following values were found:

TABLE 2 Gate output impedance, $V_{in} = 200$ mV.

	V_{out}	R_o
P87C750, EBFFA,16	154 mV	3348 Ω
P87C750, PBFFA,40	156 „	3545 „
EP87C750-4N	160 „	4000 „
P87C750 EBPN	150 „	3000 „
S87C751 4F24	172 „	6142 „
P87C748 EBFFA	158 „	3760 „
P87C750 PBFFA	164 „	4555 „

Note that R_o is between 3 and 6 k Ω , which is sufficient higher than the value of $R_1 = 100\Omega$ in fig.6. to have no influence on the transconductance value.

4. XTAL CIRCUIT PARAMETERS

4.1 Measuring method

The crystals mentioned in this report are tested on a HP 4194A impedance/phase analyser to determine the equivalent electrical data of the crystal, required for simulation of the oscillator circuit.

To carry out the measurements, following short list of test and adjustment procedures of the instruments knobs may be of assistance to start a first measurement. The object is to get an impedance/phase curve as function of frequency around the resonance points and from this to derive the main equivalent circuit parameters at such a point.

Used instrument: HP 4194A Impedance/gain-phase analyser. The equipment should be turned on fifteen minutes before to ensure warming up.

As example, the measurement was done with a 35.25 overtone crystal.

The underlined items are settings by means of pressing the mentioned button of the item block..

- 1) Check IGPB connection with plotter (Here a HP thinkjet)
- 2) Check plotting mode: Menu >> more menus >> HPIB define >> talk only >> return.
- 3) menu >> Function >> impedance >> |Z| - Φ
- 4) menu >> sweep >> lin sweep >> sweep up.
- 5) parameter >> start >> (e.g.) 20 MHz >> stop >> 40MHz >> osc level >> 0.1 Volt.
- 6) menu >> compen >> zeroshr >> zero open >> shrt ofson >> open ofson.
- 7) Now insert the crystal. Then with sweep mode >> repeat, start testing.
- 8) menu >> display >> rect X A&B
 - (sub) menu
 - 1/3 A scale log >> auto scale A
 - 2/3 B scale lin >> auto scale B
 - 3/3 unit on >> grtcl on
- 9) The display should show now a |Z| and Φ curve from 20 to 40 MHz. Then decrease the frequency range around a resonance point.
- 10) parameter >> start >> 34 MHz >> stop >> 36 MHz >> start >> 35.2 MHz >> stop >> 35.4 MHz
- 11) Repeat auto scale A and B, step 8), menu 1/3 and 2/3.
- 12) further decrease range around $F_s=35.25$ MHz >> start >> 35.24 MHz >> stop >> 35.26 MHz.
Note: before plotting, pre-set the frequency range to a range of 2, 5 or 10 units for easier read out.
- 13) Plot both the graphs >> copy
- 14) Calculating equivalent circuit parameters around the resonance point:
Menu >> more menus >> eqvckt >> CKT E >> calc EQV para >> (plot) >> copy >> display.
- 15) Both the |Z| and Φ curves as the values of the equivalent circuit components are plotted now on one A4 page, as shown in the appendix 1 for 10 different crystals and resonators.
- 16) Table3 in next section 4.2 gives a survey of the measured data values of these devices.

Oscillators on 8-bit microcontrollers (2)**Application Note
AN97090****4.2 Measuring results.****TABLE 3** Equivalent circuit parameters of some XTALS, see also appendix 1.

Nr.	Type	Mode	$F_s=1/\sqrt{LC}$	L	Ca	Rs	Cb
1	Murata, 3p, CST12.0 T	Fund.	12 MHz	45.6 μ H	4.17 pF	6.10 Ω	40.3 pF
2	Murata, 2p, CSA12MTZ	Fund.	12 MHz	47.3 μ H	4.04 pF	5.28 Ω	27.0 pF
3	Murata, 2p, CSA16MXZ	Fund.	16 MHz	602 μ H	165 fF	11.1 Ω	13.1 pF
4	XTAL, 32.768 kHz	Fund.	32.78 kHz	9.3 kH	2.54 fF	----	1.28 pF
5	XTAL, 12 MHz, Ph.	Fund.	12 MHz	8.47 mH	20.8 fF	8.20 Ω	4.85 pF
6	XTAL, 16 MHz	Fund.	16 MHz	13.05mH	7.58 fF	10.9 Ω	2.14 pF
7a	XTAL 39.13 MHz	Fundam.	13.06 MHz	11.9 mH	12.5 fF	57.8 Ω	2.86 pF
7b	„ overtone	3rd overt	39.13 MHz	16.8 mH	0.98 fF	29.6 Ω	3.24 pF
7c	„ spurious	3rd, spur.	39.24 MHz	36.6 mH	0.45 fF	72 Ω	2.81 pF
7d	„ 2nd spurious	3rd, 2spur	39.38 MHz	113 mH	0.144fF	290 Ω	2.79 pF
8a	Murata, CSA36 00MXZ	Fund. ?	12 MHz	--	--	--	--
8b	„	3rd overt.	36.0 MHz	259 μ H	75.3 fF	17.4 Ω	8.70 pF
8c	„	3rd, spur.	36.4 MHz	1.64 mH	11.7 fF	177 Ω	3.69 pF
9a	Murata, CSA39.00MXZ	Fund.?	11.05 MHz	--	--	--	--
9b	„ 3rd overtone	3rd overt.	39.00 MHz	209 μ H	80.0 fF	13.9 Ω	9.81 pF
9c	„ spurious	3rd, spur.	39.3 MHz	1.39 mH	11.8 fF	124 Ω	2.78 pF
10a	XTAL, IQD, A216	Fund.+3rd					
10b	„ 35.25 MHz	Fund.	11.77 MHz	22.1 mH	8.28 fF	302 Ω	1.78 pF
10c	„ overtone	3rd overt.	35.256MHz	29.3 mH	0.695 fF	69.1 Ω	2.19 pF
10d	„ XTAL+ 10pF//.	3rd overt	35.251MHz	29.2 mH	0.697 fF	69.6 Ω	12.24pF
10e	„ spurious	3rd, spur.	35.32MHz	112 mH	0.181 fF	282 Ω	2.03 pF

This table includes several test results for a 35MHz, third overtone XTAL from IQD (type A216) also used for the clock oscillator circuit for the 87C750 microcontroller.

After some analysis of the XTAL equivalent circuit parameters of the available XTAL samples and the typical gain and output characteristics of the microcontroller gate, the next chapter of this application note describes several circuit proposals for the P87C750 circuit to obtain optimum start up action and to prevent oscillation in the undesirable fundamental mode.

5. CRYSTAL OVERTONE OSCILLATOR

This chapter gives some application proposals for 3rd overtone XTAL circuits, used for the clock generation section of microcontrollers .

For these applications, precautions should be taken to prevent oscillation in the fundamental mode and to force the overtone mode.


Three proposals are given:

- 1) Higher damping of the fundamental mode by applying a low ohmic resistor across the gate.
- 2) Connection of an inductor L between gate output and ground to trap the fundamental mode
- 3) Connection of such an inductor between the gate input and ground.

For clock frequencies in excess of 15 to 20 MHz, standard XTALs are not preferred or available and the overtone oscillation mode should be used.

Following some circuit possibilities for such a XTAL for 39 MHz clock generation for a P87C750 microcontroller are given.

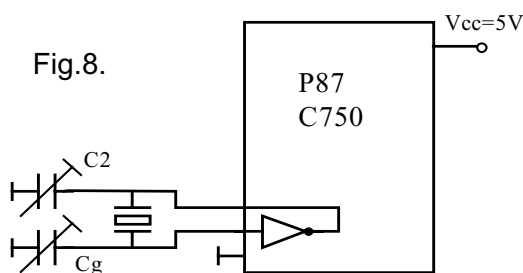A circuit diagram of the oscillator with the internal gate of the micro is given in Fig. 8.



The circuit above, together with the 3rd overtone XTAL, only oscillates at its fundamental mode. Hence measures are required to force the circuit into the third overtone mode.

The equivalent XTAL circuit data, as shown in Fig.9b, are listed below for the fundamental mode and for the third overtone.

XTAL 39.13 MHz 3rd overtone

Mode	Fseries	L	Ca	Rs	Cb
First	13.05 MHz	11.9 mH	12.5 fF	57.6 Ω	2.84 pF
Third	39.13 MHz	16.4 mH	1.0 fF	30.3 Ω	3.34 pF
Third (Spur.)	39.24 MHz	33.6 mH	0.45 fF	72 Ω	2.8 pF


For this XTAL, the ratio $R_{s_1}/R_{s_3} = 57.6 / 30.3 = 1.9$.

For the A216, $R_{s_1}/R_{s_3} = 4.3$ See chapter 4

Based upon these results for the XTAL parameters, next section will discuss the results of some practical tests with the XTALs used with the microcontroller circuit.

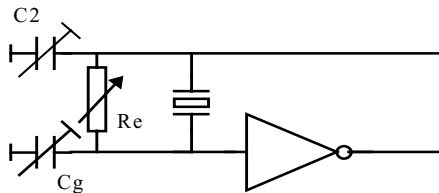5.1 Forcing overtone mode by frequency dependent damping.

This circuit uses a low value resistance between gate output and input. See Fig.2a



$C_g=4.7\text{pF}$, $C_2=15\text{pF}$, $R_e=3900\text{ Ohm}$.

Fig.9a

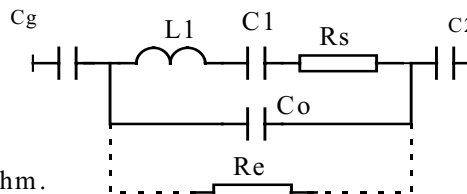


Fig.9b

Forcing the third overtone mode can be achieved by connecting a low ohmic resistor R_e in parallel with the XTAL. Fig. 2b shows the equivalent XTAL circuit diagram with R_e connected and C_p as the total parallel capacitance to the XTAL, $C_p= C_o + C_gC_2/(C_g+C_2)$.

This circuit will oscillate either in fundamental mode or in 3rd overtone, if the gate amplifier compensates for the damping by resistors R_s and external R_e . But damping influence of R_e is much higher for the fundamental mode, which can be shown by replacing R_e into the series loop of $L_1/C_1/R_s$ and C_o as R_{e_s} .

$$\text{This delivers : } R_{e_s} = \frac{1}{\omega^2 C_p^2 R_e}$$

This equation shows that R_e has a 9 times lower damping value into the series resonance circuit at the requested overtone frequency.

With the above specified XTAL and the gate of a microcontroller P87C750 (PBFFA), this circuit has been tested and proved to oscillate at the third overtone at all conditions with the following circuit values:

XTAL: 39.13MHz, $C_g=4.7\text{pF}$, $C_2=15\text{pF}$, $R_e= 3900\text{ Ohm}$.

5.2 Connection of a inductive trap filter to the output.

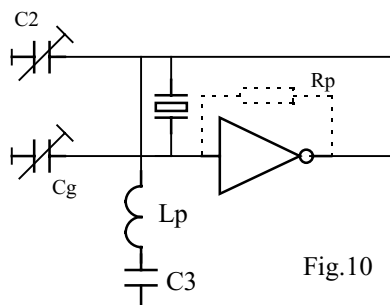


Fig.10

$C_g=10\text{ pF}$
 $C_2=27\text{ pF}$
 $L_p= 1.5\text{ microH.}$
 $C_3= 4700\text{ pF}$

In this circuit, the fundamental mode is suppressed by connecting an inductance L to the output of the gate amplifier. Together with a part of the capacitance C_2 at the output, this inductor will perform a high impedance parallel circuit at the overtone frequency and a low inductive impedance at the fundamental one. The capacitance C_3 is a DC decoupling capacitor for the gate bias voltage, sourced by the (internal) resistor R_p . With $L_p=1.5\text{ microH}$, resonance at 39 MHz occurs with $C_2= 1/(\omega^2 L) = 11\text{pF}$. Hence, the value of C_2 should be $>11\text{pF}$. In the practical test, correct overtone oscillation was obtained with the following circuit values:

$C_g= 10\text{ pF}$, $C_2= 27\text{ pF}$, $L_p = 1.5\text{ microH.}$ and $C_3= 4700\text{ pF}$.

5.3 Inductive filter at the input.

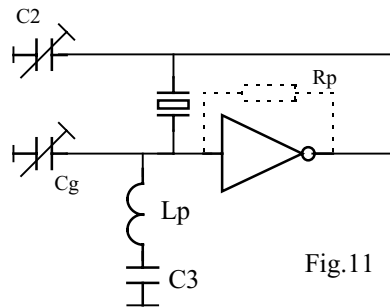


Fig.11

$C_g = 10 \text{ pF}$
 $C_2 = 10 \text{ pF}$
 $L_p = 1.5 \text{ microH.}$
 $C_3 = 4700 \text{ pF}$

Here the inductive trap filter is connected at the input side. Optimum circuit values for this case were: $C_g=10\text{pF}$, $C_2=10\text{pF}$, $L_1=1.5\text{microH}$ and $C_3=4700\text{pF}$.

Hence at 39MHz the capacitance C_g is fully tuned out by L_p , the only capacitance left at the input is the input stray and pin capacitance, in the order of 5pF.

Note.

The circuit values given above are the optimal values for the applied XTAL as specified above and a typical microcontroller oscillator gate, with a measured transconductance, at $V_{cc}=5\text{V.}$, of around 4.5 mA/V.

Other values may be required with other devices.

For these excersices several measurements have been done to determine the properties of the used XTAL and the current gain (transconductance) of the oscillator gate of the microcontroller. The parameters of the crystal and the inverter-gate together determine the correct oscillation mode of the circuit and its start-up behaviour.

5.4 Drive level.

At high frequencies, drive levels are increased due to the low impedance of C_o . The drive level is given by the power, dissipated in the series resistance R_s of the XTAL. Hence $P_d = I_s^2 \cdot R_s$. At resonance, the current I_s in the series branch is equal to the current through C_o , the total parallel capacitance in the circuit, see Fig.2. At $V_{cc}=5\text{V}$, the peak to peak voltage at both sides of the XTAL is 5 Volts, but inverted. Hence the peak voltage across the XTAL and C_o is 5Volt and the effective voltage V_x is $5\text{V}/\sqrt{2}$, or $V_x=3.5\text{V}$. Then, $I_s = V_x \cdot \omega C_o$, or $P_d = (V_x \cdot \omega C_o)^2 \cdot R_s$.

With $C_o=C_{load}=18\text{pF}$, $\omega=2\pi \cdot 35\text{e}6$ and $R_s=69\Omega$, $P_d = (3.5 \times 2\pi \cdot 35\text{e}6 \times 18\text{e-}12)^2 \cdot 69 = 13 \text{ mW}$. This is far above the recommended drive level as specified for the A216 XTAL, $P_{dmax}=500\mu\text{W}$.

Hence P_d should be reduced, by selecting a lower value for C_{load} . With $C_1=C_2=4.7\text{pF}$, $C_{load}=3\text{pF}$, and the value of C_o is about 5pF. This will reduce P_d to around 1mW, which would be a safe value for P_d to prevent intensified ageing.

5.5 Conclusion.

From the practical test with a typical sample of an overtone XTAL and a 87C750 microcontroller, it was found that the specified load capacitance is a too high value to get correct working of the clock oscillator. With the

given circuits, a good start up condition in the desired overtone mode was obtained with a reduced load capacitance, e.g. $C1 = 4.7\text{pF}$ at the input and $C2 = 4.7\text{pF}$ (or up to 10pF) at the output side of the XTAL,.

For worst case operation with suppression of the fundamental mode of operation, it may be recommended to use an inductive trap filter for the low frequency, e.g. by connecting $L = 1.5\mu\text{H}$, in series with $Cs = 4.7\text{nF}$, from output to ground with $C1 = 4.7\text{pF}$ and $C2 = 22\text{pF}$.

6. MURATA CERAMIC RESONATORS

An alternative to the traditionally used quartz crystal resonator is the ceramic resonator. The disadvantage of the ceramic resonator is the lower frequency accuracy. If an microcontroller application needs for some reason a very accurate timing then a quartz crystal is usually the only option. For many microcontroller applications timing issues may however be less critical and the ceramic resonator will be an excellent replacement.

A ceramic resonator has several strong advantages:

- lower price
- not sensitive for drive level
- no additional components required for higher frequency (overtone).
- better (mechanical) shock resistance

Microcontrollers are also available for very low cost applications requiring suitable resonators. The muRata company has an excellent reputation in ceramic technology and is offering several ranges of resonators.

For many IC's a suitable resonator can be found in the product programme. Following issues are dedicated to 8-bit microcontroller types.

6.1 Resonator types for 8400 and 8051 microcontrollers

Following table lists a number of PHILIPS SEMICONDUCTOR microcontroller types that were evaluated by muRata with muRata type resonators. These resonator types provide reliable oscillation with the microcontroller types involved.

An external feedback resistor (R_f) that is normally required for an feedback when using an unbuffered CMOS gate can be omitted in most cases because it is integrated in most microcontroller oscillator inverters.

MICROCONTROLLER	CERALOCK	CL1[pF]	CL2[pF]	Rf[ohm]	Rd[ohm]
87C51FA	CSACS24.00MX040	5	5	Open	0
87C51FA	CSTCS24.00MX0H1	5	5	Open	0
87C750	CSTCC6.00MGA0H6	0	0	Open	0
P80C52	CSA12.0MTZA	30	30	Open	0
P80C52	CST12.0MTWA	30	30	Open	0
P80C851FBA	CSTCS12.0MT	0	0	Open	0
P80CL51	CSTCC3.68MG0H6	0	0	Open	0
P80CL51HFT	CSB1000J	100	100	Open	5.6k
P80CL782	CSAC6.00MGC	30	30	Open	0
P80LC51HFP	CSA10.0MTZ	30	30	Open	0
P80LC51HFP	CSA3.58MG	30	30	Open	0
P80LC51HFP	CST10.0MTW	30	30	Open	0
P80LC51HFP	CST3.58MGW	30	30	Open	0
P80LC51HFT	CSA10.0MTZ	30	30	Open	0
P80LC51HFT	CSA3.58MG	30	30	Open	0
P80LC51HFT	CST10.0MTW	30	30	Open	0
P80LC51HFT	CST3.58MGW	30	30	Open	0

Oscillators on 8-bit microcontrollers (2)**Application Note
AN97090**

P83C575EHP	CST6.29MGWHA	30	30	Open	0
P83C749EFPN	CSA16.00MXZA040	15	15	Open	0
P83C750	CSA12.0MTZ	30	30	1M	0
P83C750	CST12.0MTW	30	30	1M	0
P84C84X	CSA10.0MTZ	30	30	Open	0
P84C84X	CST10.0MTW	30	30	Open	0
P87C52	CSA24.00MXZ040	10	10	1M	0
P87C52EBPN	CSA16.00MXZ040	15	15	Open	0
P87C52EBPN	CSA20.00MXZ040	10	10	1M	0
P87C54IBAA	CSA12.0MTZ	30	30	Open	0
P89CE558EFB	CST12.0MTWA	0	0	Open	0
PCF80C552-4	CST11.0MT020	30	30	Open	0
PCF80C562	CSACS11.0MTA	30	30	Open	0
PCF84C00B	CSA6.00MG097	0	0	Open	0
PCF84C12	CSA3.58MG310VA	0	0	Open	0
PCF84C21	CSA3.00MG	30	30	1M	0
PCF84C21	CST3.00MGW	30	30	1M	0
PCF84C22	CSA6.00MGA013	0	0	Open	0
PCF84C270	CSA3.58MG310VA	0	0	Open	0
PCF84C444	CSA8.00MTZ	30	30	Open	0
MICROCONTROLLER	CERALOCK	CL1[pF]	CL2[pF]	Rf[ohm]	Rd[ohm]
PCF84C81AP	CST6.00MGW	30	30	Open	0
S87C51FB	CSA12.0MTZ	30	30	Open	0
S87C51FB	CST16.00MXW0C3	0	0	Open	0
S87C652	CSA10.0MTZ	30	30	Open	0
S87C652	CSACS18.43MX040	10	10	Open	0
S87C654	CSA12.0MTZ	30	30	Open	0
S87C751	CSA3.58MG	30	30	Open	0
S87C751	CSAC11.9MT	30	30	Open	0
S87C751	CSACS16.00MX040	15	15	Open	0
S87C751	CST3.58MGW	30	30	Open	0
S87C751	CSTCS16.00MX0C3	15	15	Open	0

6.2 Resonator types for the P87CL884

Recently the P87CL884 was also evaluated by muRata for several frequencies and resonator giving the following results:

6.2.1 1...8 Mhz types

1.00MHz CSB1000J	with CL1=CL2 = 100pF	Rd = 4.7kOhm	Rf open
2.00MHz CSA2.00MG	with CL1=CL2 = 30pF	Rd = 0	Rf open
2.00MHz CST2.00MG	with CL1=CL2 = 30pF(internal)	Rd = 0	Rf open
3.58MHz CSA3.58MG300ABC	with CL1=CL2 = 30pF	Rd = 0	Rf open
3.58MHz CST3.58MGW300ABC	with CL1=CL2 = 30pF	Rd = 0	Rf open
4.00MHz CSA4.00MG	with CL1=CL2 = 30pF	Rd = 0	Rf open
4.00MHz CST4.00MGW	with CL1=CL2 = 30pF(internal)	Rd = 0	Rf open
8.00MHz CSA8.00MT093	with CL1=CL2 = 30pF	Rd = 0	Rf open
8.00MHz CST8.00MTZ093	with CL1=CL2 = 30pF(internal)	Rd = 0	Rf open

6.2.2 12...20 Mhz resonators

With these frequencies the oscillator signal level was so small that no signal could be detected at the clock out pin (pin18).

For this reason it is NOT recommended to use ceramic resonators on these frequencies.

6.2.3 3.58 Mhz resonators

Resonator with frequency of 3.58 Mhz are in the 300 series. These series are optimised for use with DTMF IC's. These resonators have smaller tolerances on their frequency to match the DTMF specification requirements.

6.3 Resonator types for the P80C54/P87C51RA+

The PHILIPS SEMICONDUCTOR microcontroller products are continually improved by new technologies.


The latest versions of the 80C54 and the 87C51RA+ were also evaluated by muRata with the resonator types: CSA16.00MXZ040 and CST16.00MXW0C3. Results are documented in a report by muRata (see ref. 6)

7. REFERENCES

1. AN 96103. XTAL oscillators on 8-Bit microcontrollers. Application note, André Pauptit.
2. ETT8710 Specification of Quartz and ceramic resonators. Lab. report, Jaap Mulder.
3. Techn. note: Start-up conditions for Quartz crystal and PXE oscillators. Nov. 1989. W.Thommen
4. IEEE Tr. on circuits. Start-up condition of CMOS oscillators. march 87, no.3. Andreas Rusznyak.
5. AN 456. Using LC oscillators with Philips microcontrollers. William Houghton.
6. Technical Data of Ceramic Resonator, TCD No.TCD-97-5o04, Toyama muRata manufacturing Co,Ltd.


7.1 Appendix

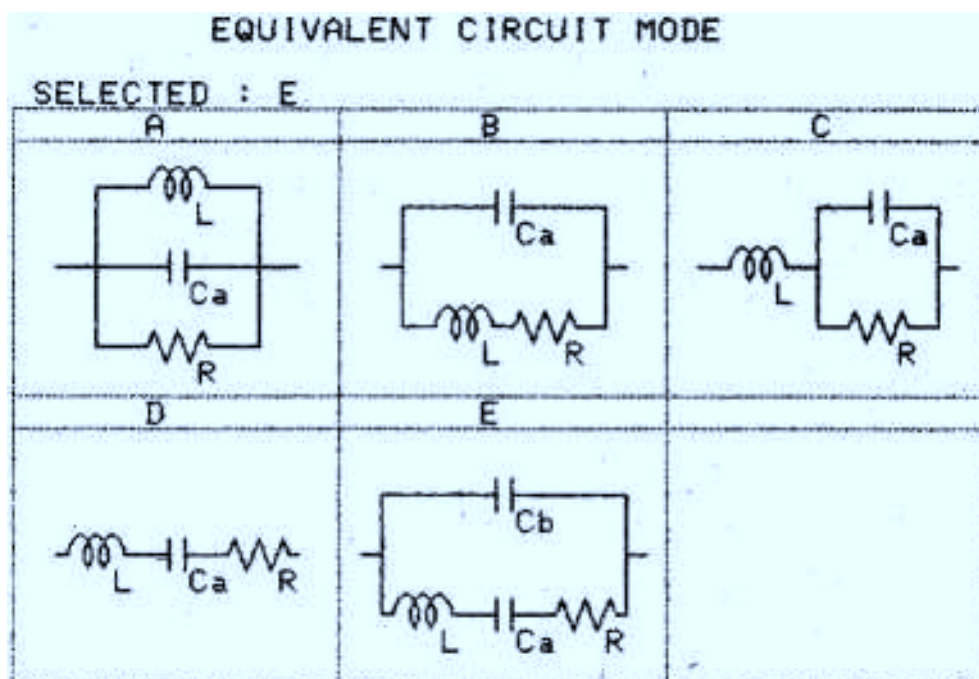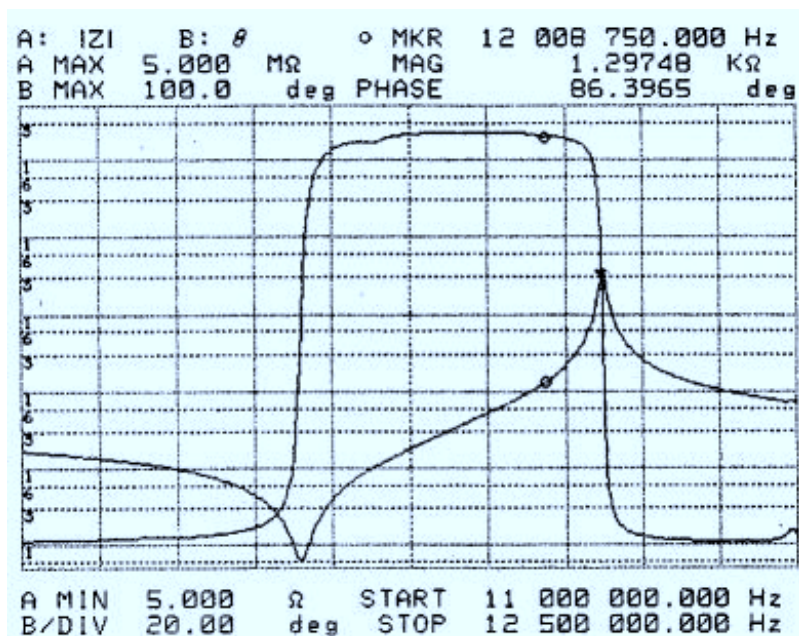The following equivalent circuit diagrams apply to all figures in the appendix. The relevant values for R, L, Ca and Cb are listed there (R in Ohm, L in μH and C in pF).

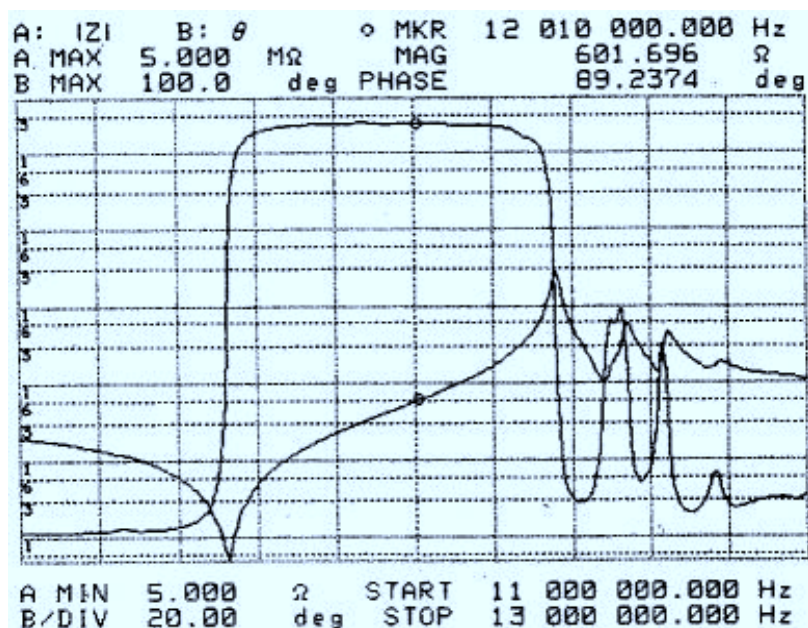


App. 0

Oscillators on 8-bit microcontrollers (2)

Application Note
AN97090


App 1

Resonator Murata, 3 pins, CST 12.0T, $F_S=12.0$ MHz $R = 6.10535 \Omega$ $C_a = 4.17542$ pF $L = 45.5682 \mu\text{H}$ $C_b = 40.2569$ pF


App 2

Resonator Murata, 2 pins, CSA 12.0MTZ, $F_S=12.0$ MHz $R = 5.28065 \Omega$ $C_a = 4.03804$ pF $L = 47.2664 \mu\text{H}$ $C_b = 27.0237$ pF

Oscillators on 8-bit microcontrollers (2)

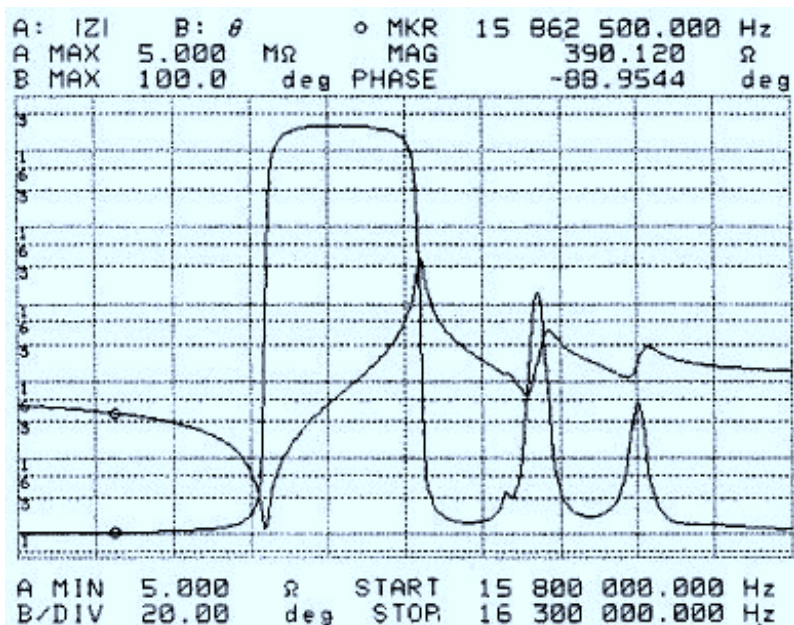Application Note
AN97090

App 3

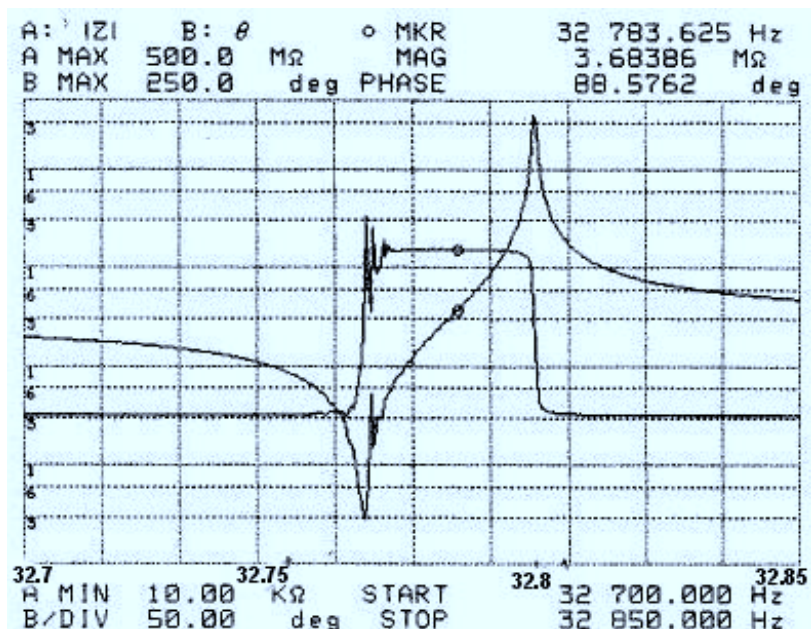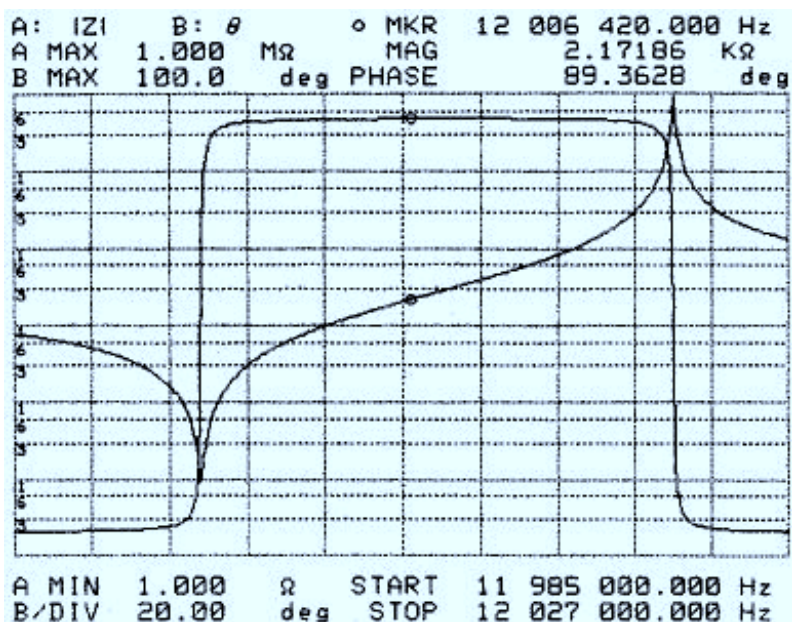
Resonator Murata, 2 pins, CSA 16.0MX, $F_s=16.0$ MHz $R = 11.0840 \Omega$ $C_a = 165.139$ fF $L = 602.177$ μ H $C_b = 13.0631$ pF

App 4


Resonator 32.768 kHz

 $R = 0 \Omega$ $C_a = 2.54110$ fF $L = 9.28503$ kH $C_b = 1.27633$ pF

Oscillators on 8-bit microcontrollers (2)

Application Note
AN97090


App 5

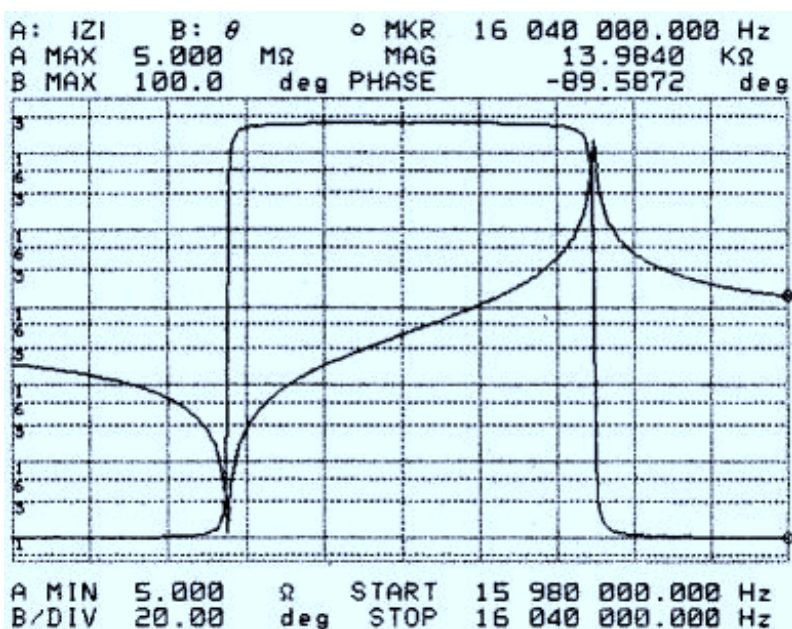Crystal Philips, 12000.000 code 4631.024, $F_s=12$ MHz $R = 8.19832 \Omega$ $C_a = 20.7893$ fF $L = 8.46836$ mH $C_b = 4.85404$ pF

App 6

Crystal Philips, 16000.000 code 200002.017, $F_s=16$ MHz $R = 10.8692 \Omega$ $C_a = 7.58601$ fF $L = 13.0490$ mH $C_b = 2.13657$ pF

Oscillators on 8-bit microcontrollers (2)

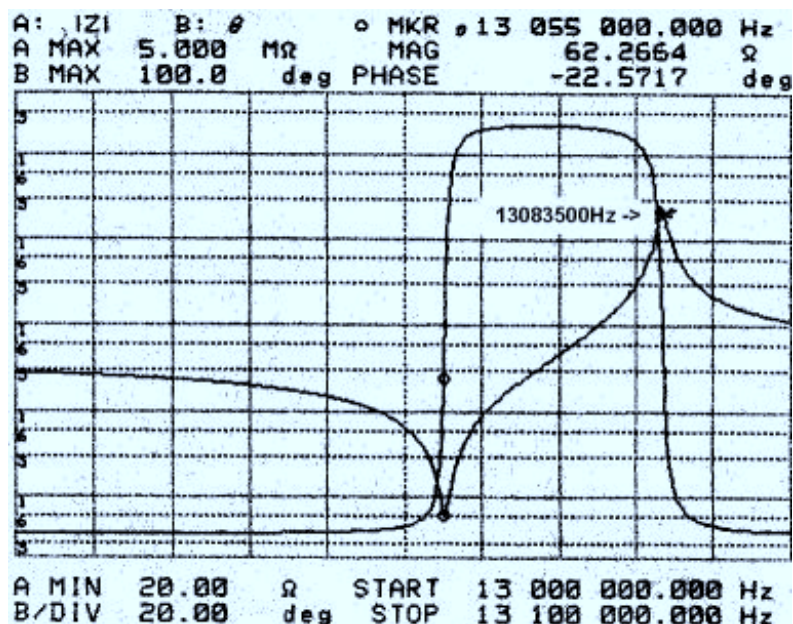Application Note
AN97090

App 7a


Crystal Philips 3rd overtone. Code 02370991. $F_s = 39.130000$ MHz
 Response at fundamental frequency, $F = 13.05$ MHz

$R = 57.8032 \Omega$

$C_a = 12.4900$ fF

$L = 11.8991$ mH

$C_b = 2.86327$ pF

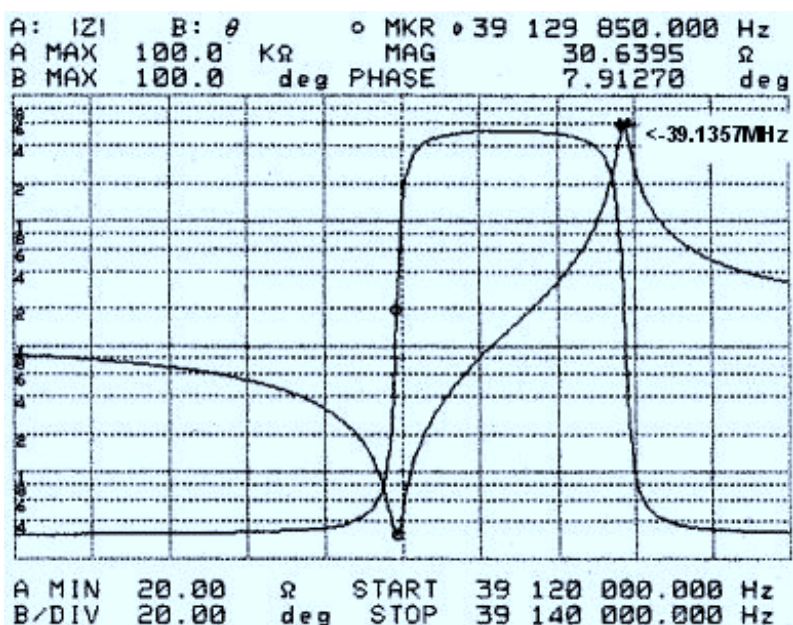

App 7b

Crystal Philips 3rd overtone. Code 02370991. $F_s = 39.130000$ MHz
 Response at 3rd overtone, $F = 39.13$ MHz


$R = 29.5671 \Omega$

$C_a = 0.983545$ fF

$L = 16.8202$ mH

$C_b = 3.24510$ pF

Oscillators on 8-bit microcontrollers (2)

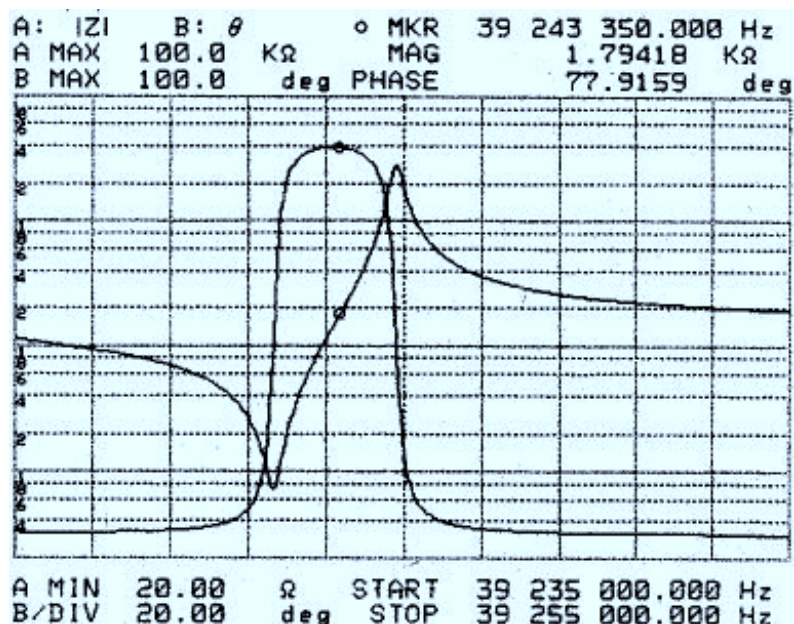Application Note
AN97090

App 7c


Crystal Philips 3rd overtone. Code 02370991. $F_s = 39.130000$ MHz
 Response 3rd overtone frequency, spurious $F = 39.24$ MHz

$R = 72.0326 \Omega$

$C_a = 0.448987$ fF

$L = 36.6363$ mH

$C_b = 2.80858$ pF

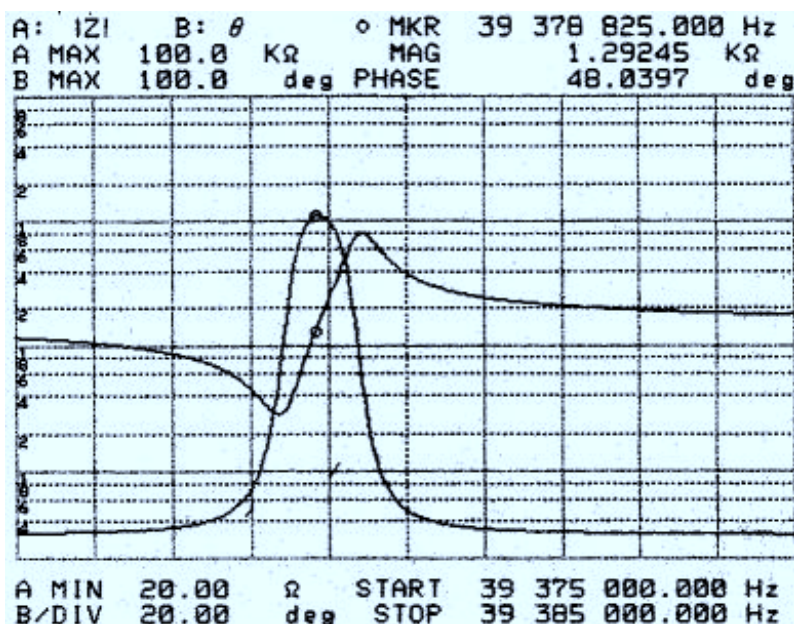

App 7d

Crystal Philips 3rd overtone. Code 02370991. $F_s = 39.130000$ MHz
 Response at 3rd overtone, 2nd spurious $F = 39.38$ MHz



$R = 290.131 \Omega$

$C_a = 0.144278$ fF

$L = 113.220$ mH

$C_b = 2.79147$ pF


Oscillators on 8-bit microcontrollers (2)

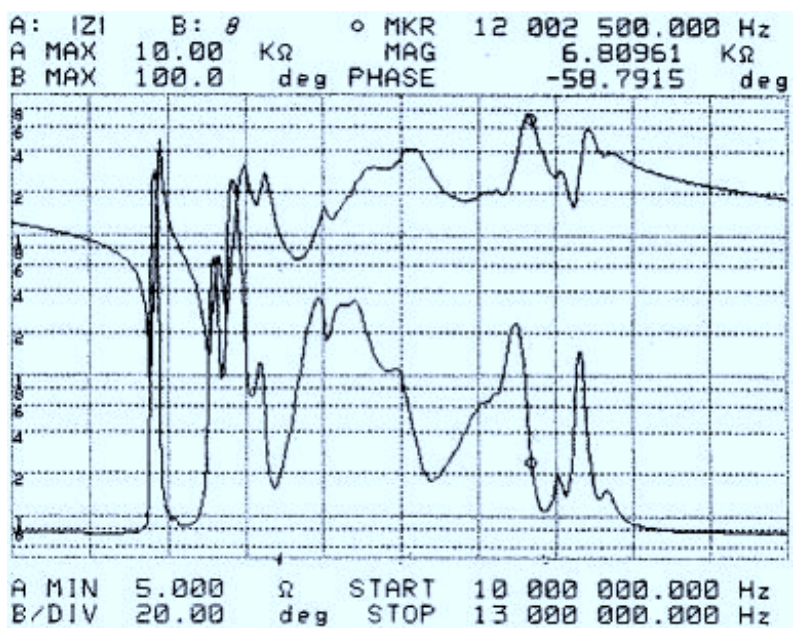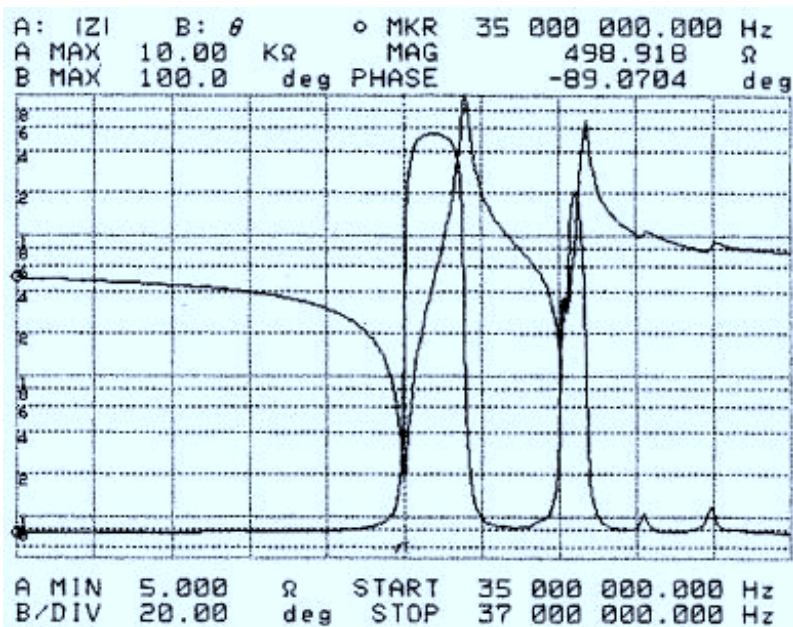Application Note
AN97090

App 8a

Resonator, Murata, 3rd overtone, CSA 36.00 MXZ 040, F_s =36 MHz.
 Response at 3rd overtone and around fundamental, 36 MHz and 12 MHz

Oscillators on 8-bit microcontrollers (2)

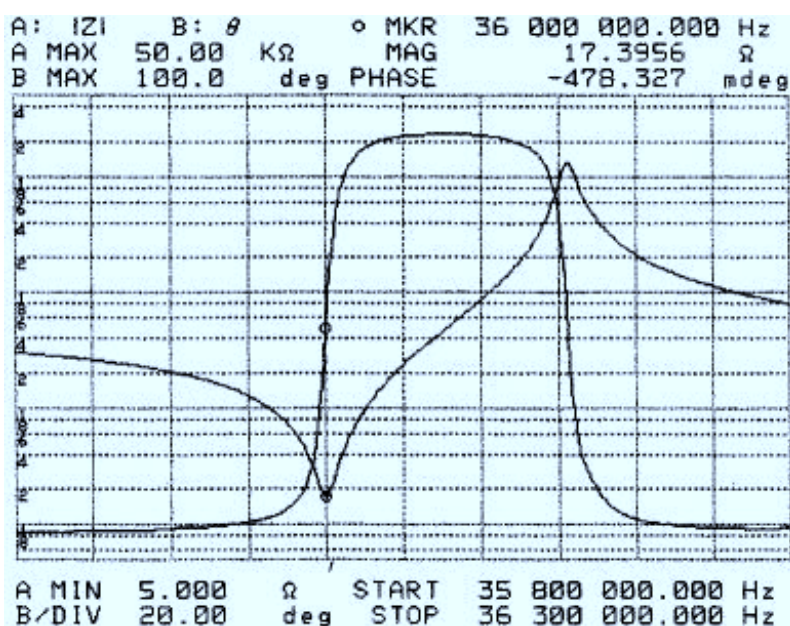Application Note
AN97090


App 8b Resonator, Murata, 3rd overtone, CSA 36.00 MXZ 040, F_s =36 MHz.
 Response at 3rd overtone 36 MHz

$R = 17.4101 \Omega$

$C_a = 75.3167 \text{ fF}$

$L = 259.506 \mu\text{H}$

$C_b = 8.69794 \text{ pF}$

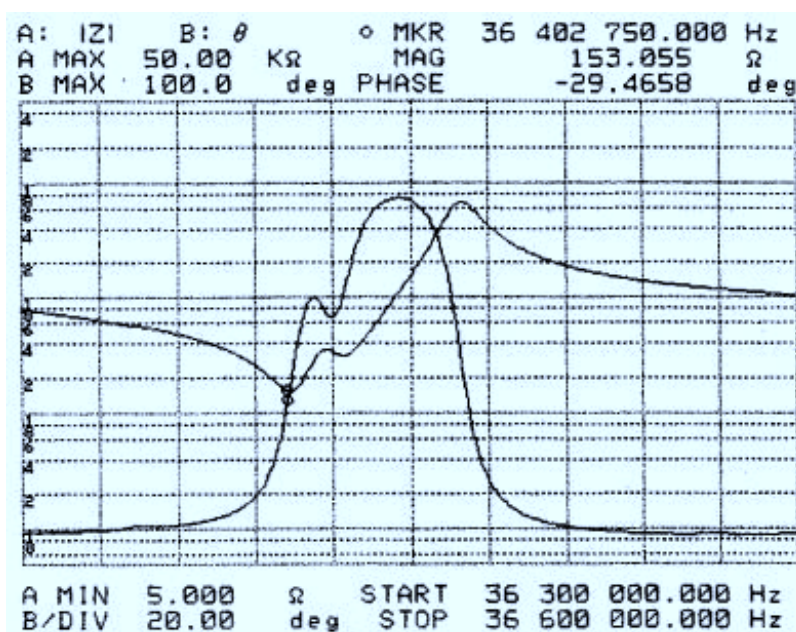



App 8c Resonator, Murata, 3rd overtone, CSA 36.00 MXZ 040, F_s =36 MHz.
 Response at 3rd overtone spurious frequency 36.4 MHz

$R = 177.476 \Omega$

$C_a = 11.6752 \text{ fF}$

$L = 1.63697 \text{ mH}$


$C_b = 3.69068 \text{ pF}$

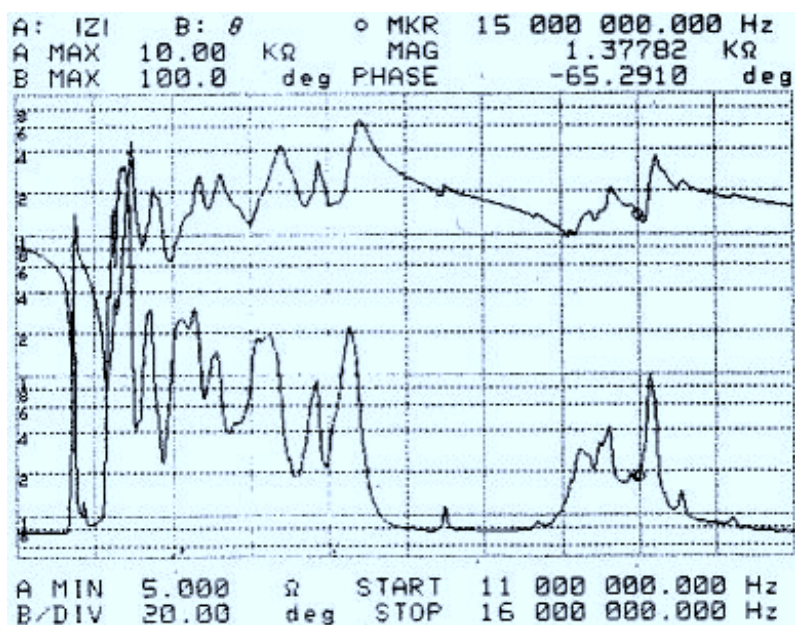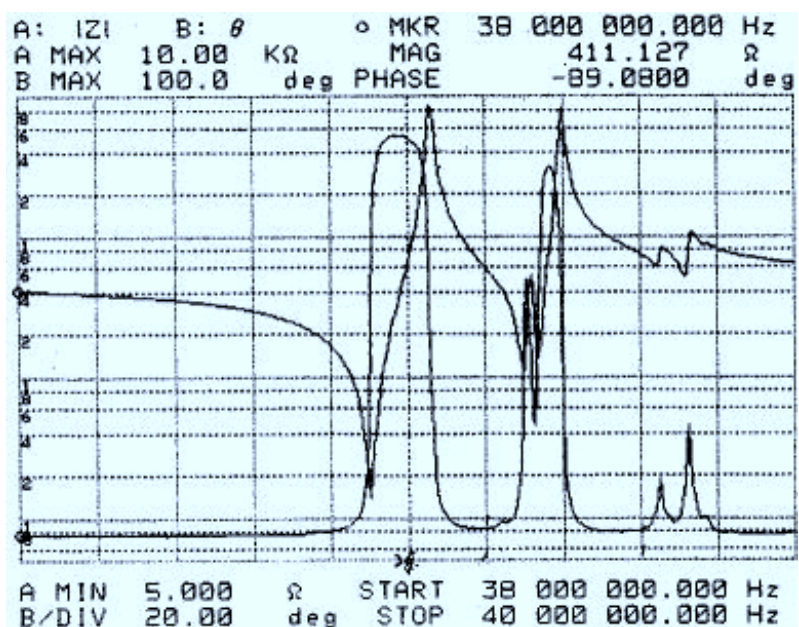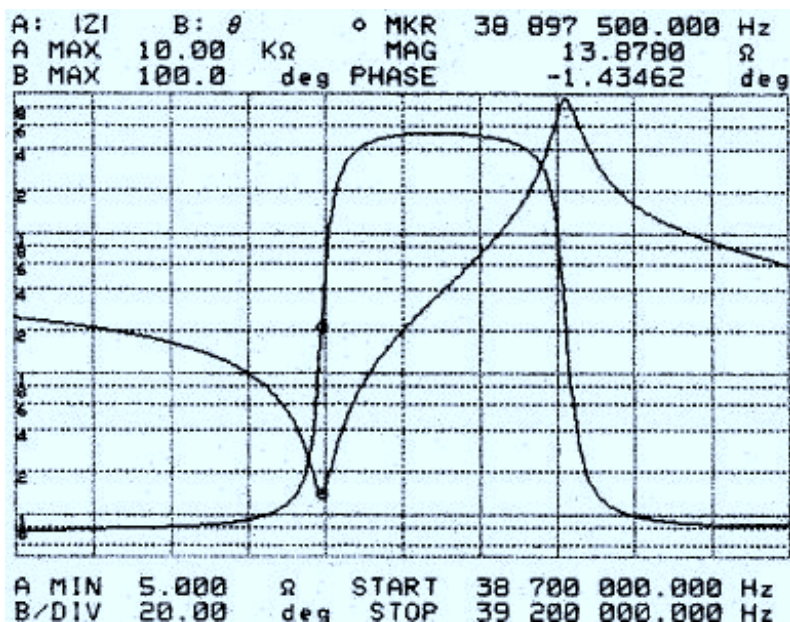

App 9a

Resonator, Murata, 3rd overtone, CSA 39.00 MXZ 040, F_s =39 MHz.
 Response at 3rd overtone and around fundamental, 39 MHz and 13 MHz

Oscillators on 8-bit microcontrollers (2)

Application Note
AN97090


App 9b Resonator, 3rd overtone, CSA 39.00 MXZ 040, $F_s=39$ MHz.
Response at 3rd overtone 38.9 MHz

$R = 13.8946 \Omega$

$C_a = 79.9597 \text{ fF}$

$L = 209.376 \mu\text{H}$

$C_b = 9.81582 \text{ pF}$

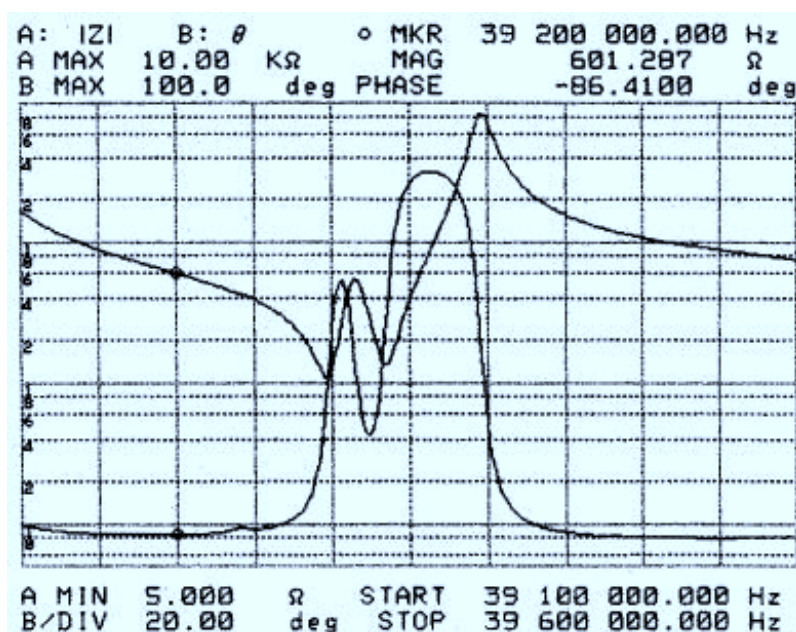

App 9c Resonator, 3rd overtone, CSA 36.00 MXZ 040, $F_s=39$ MHz.
Response at 3rd overtone 39.3 MHz



$R = 124.243 \Omega$

$C_a = 11.7911 \text{ fF}$

$L = 1.39105 \text{ mH}$

$C_b = 2.78760 \text{ pF}$


Oscillators on 8-bit microcontrollers (2)

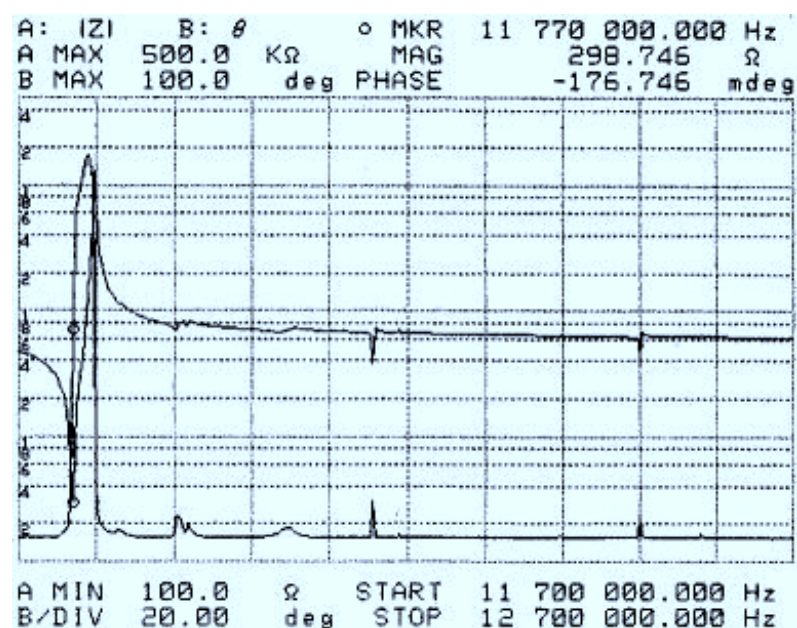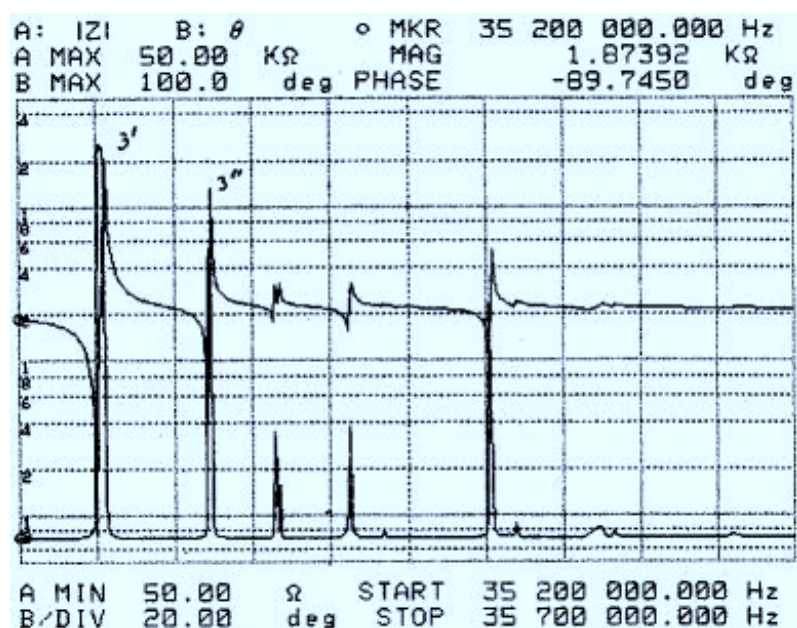Application Note
AN97090


App 10a

Crystal IQD. A216, 3rd overtone. F_s =35.2512 MHz. Response around overtone and fundamental frequencies, 35.2 MHz and 11.7 MHz

Oscillators on 8-bit microcontrollers (2)

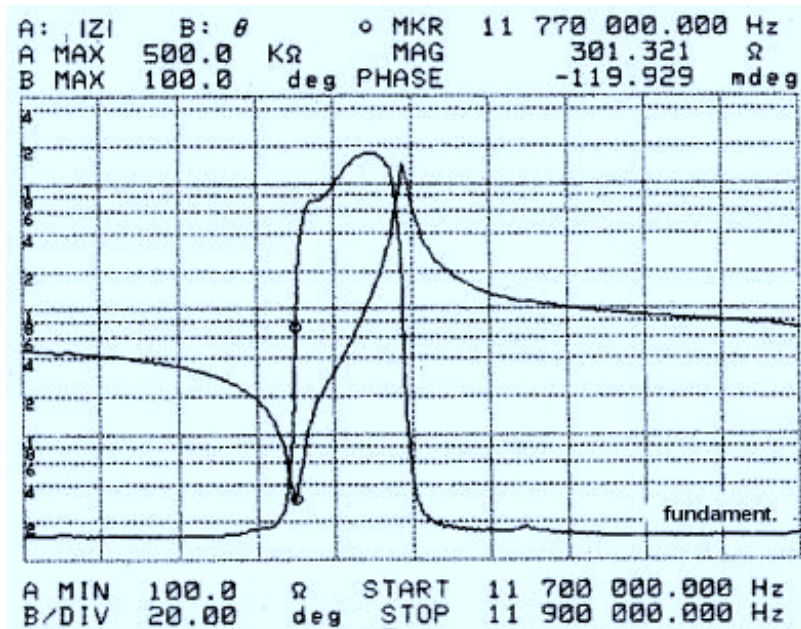Application Note
AN97090


App 10b

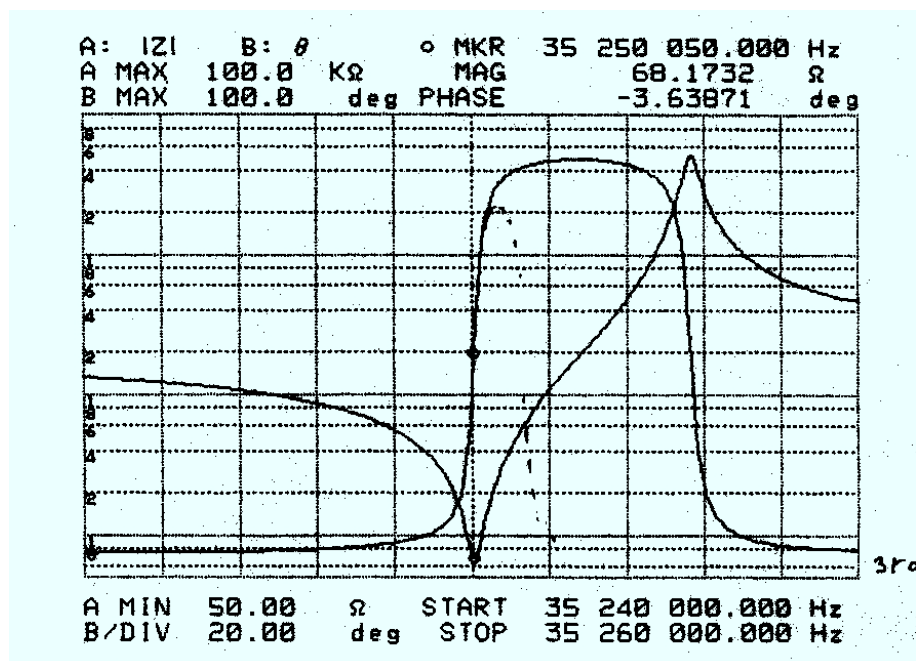Crystal IQD. A216, 3rd overtone. $F_s=35.2512$ MHz. Response at fundamental frequency, $F=11.77$ MHz $R = 302.660 \Omega$ $C_a = 8.28450$ fF $L = 22.0710$ mH $C_b = 1.78188$ pF

App 10c

Crystal IQD. A216, 3rd overtone. $F_s=35.2512$ MHz. Response at 3rd overtone, $F_P=35.256$ MHz $R = 69.0873 \Omega$ $C_a = 0.695554$ fF $L = 29.3083$ mH $C_b = 2.19626$ pF

Oscillators on 8-bit microcontrollers (2)

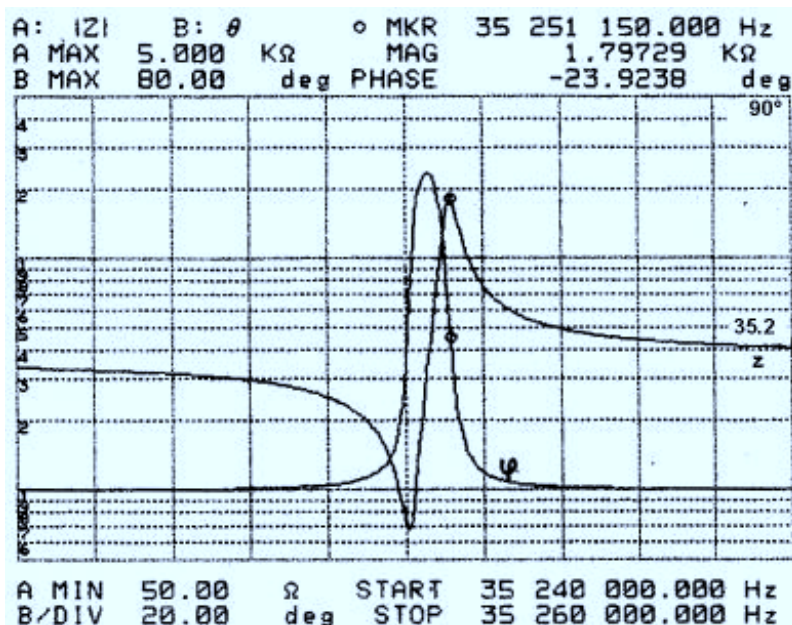Application Note
AN97090

App 10d


Crystal IQD. A216, 3rd overtone. $F_s=35.2512$ MHz. Response at 3rd overtone, 10pF load added in parallel to crystal. $F=35.251$ MHz

R = 69.6577 Ω

Ca = 0.697244 fF

L = 29.2372 mH

Cb = 12.2397 pF

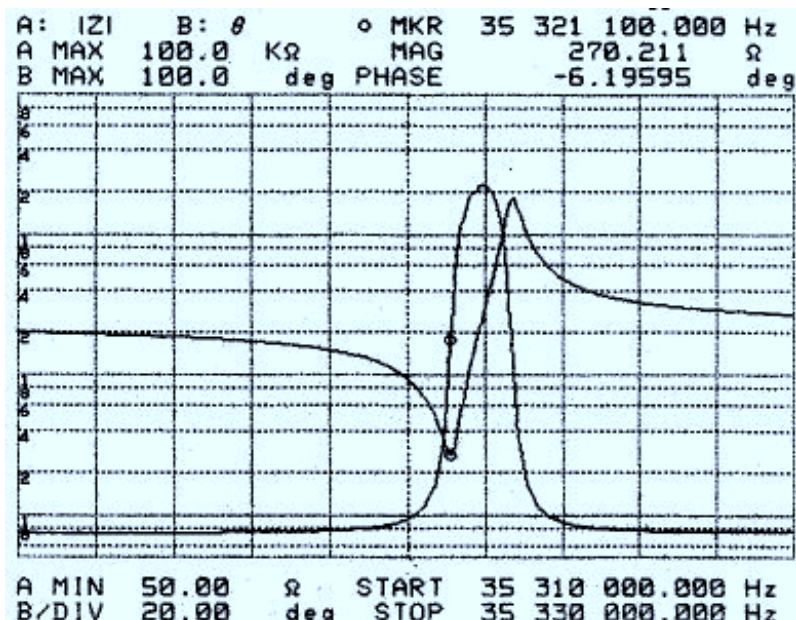

App 10e

Crystal IQD. A216, 3rd overtone. $F_s=35.2512$ MHz. Response at 3rd overtone, spurious frequency, $F=35.32$ MHz

R = 282.210 Ω

Ca = 0.180806 fF

L = 112.295 mH

Cb = 2.02789 pF